

1.1 Polyphase Circuits

JUAN MANUEL REY LÓPEZ
Profesor Auxiliar
juanmrey@uis.edu.co

Escuela de Ingenierías Eléctrica, Electrónica y de
Telecomunicaciones
Universidad Industrial de Santander



I - 2015

C O N S T R U I M O S F U T U R O


Universidad
Industrial de
Santander




¿Polyphase circuits?

- «Polyphase circuits / systems : in which AC sources operate at the same frequency but different phase» [Sadiku]


Polyphase circuits

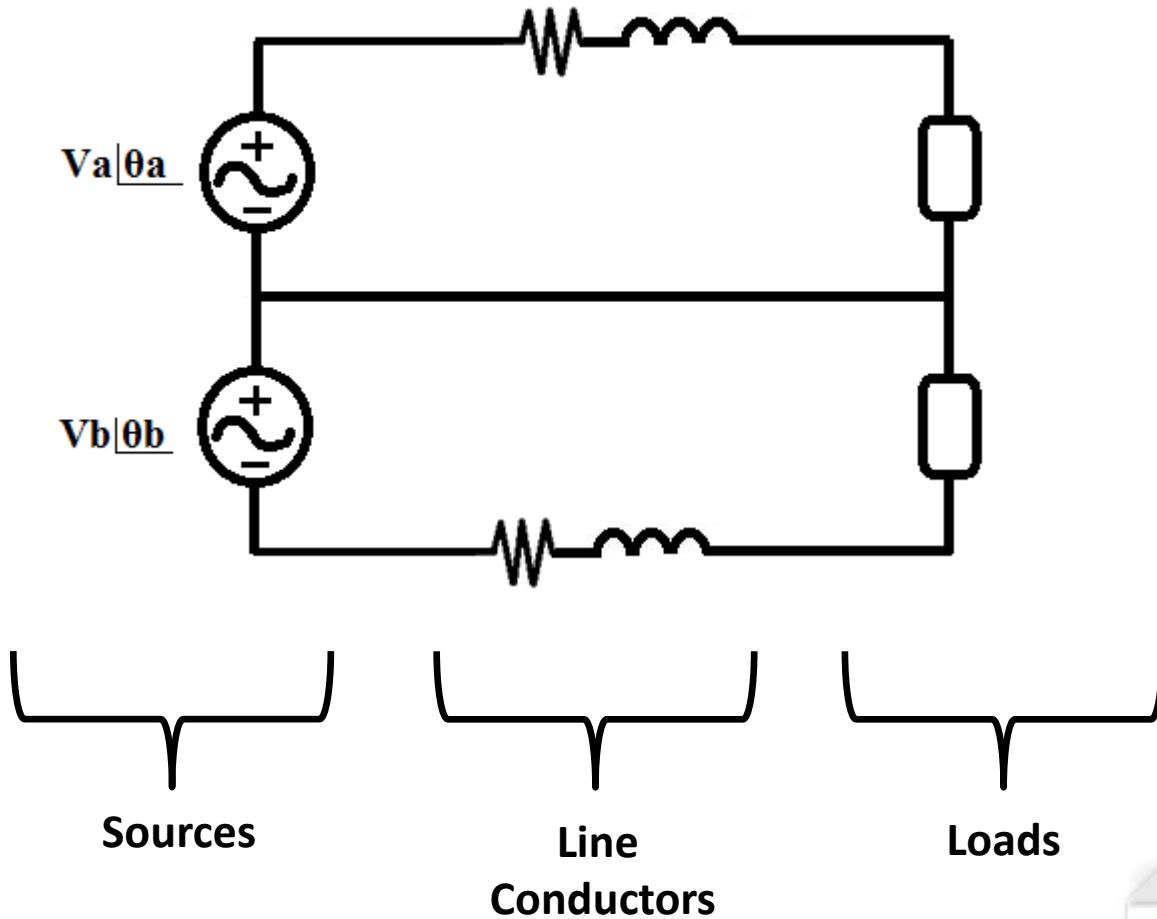


Single-phase circuits

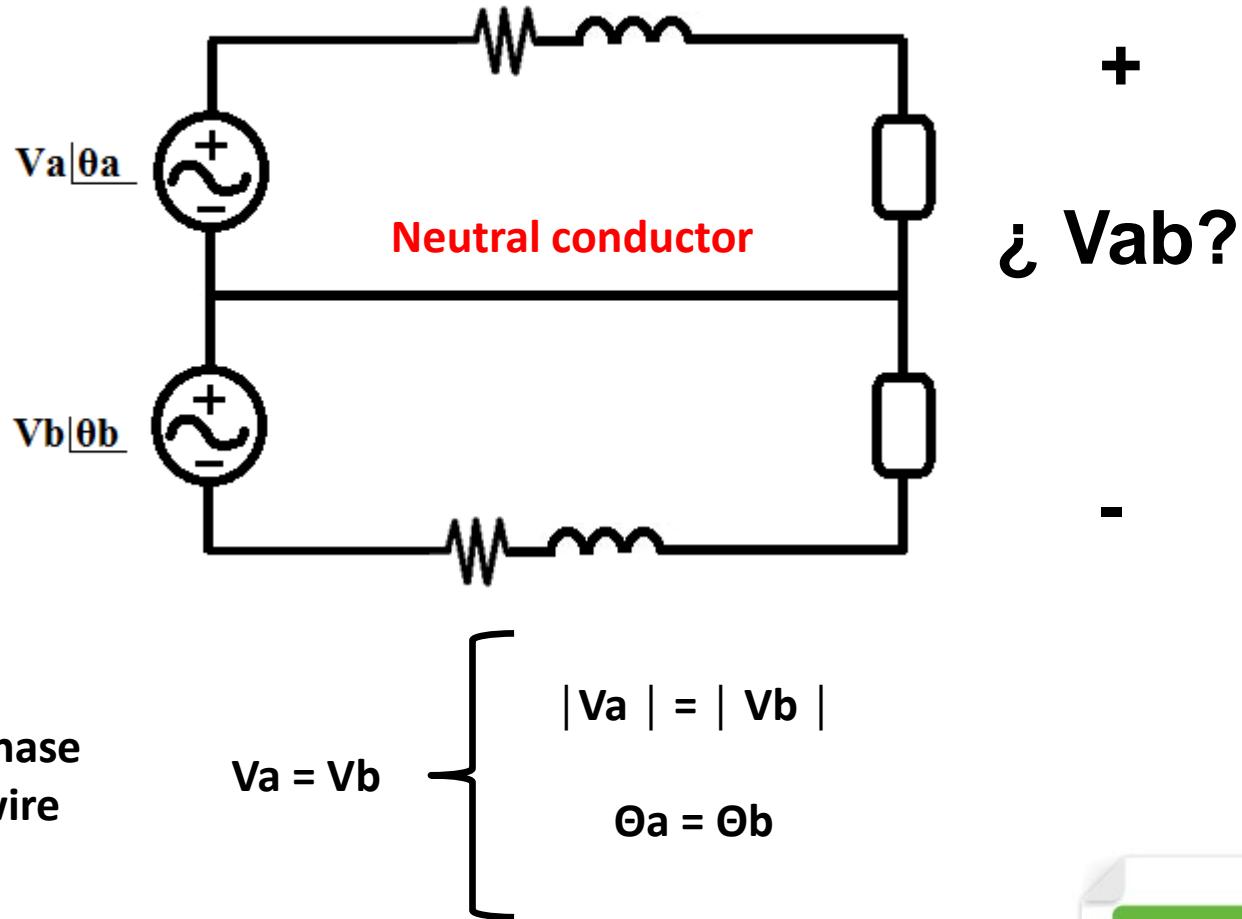

Bi-phase circuits

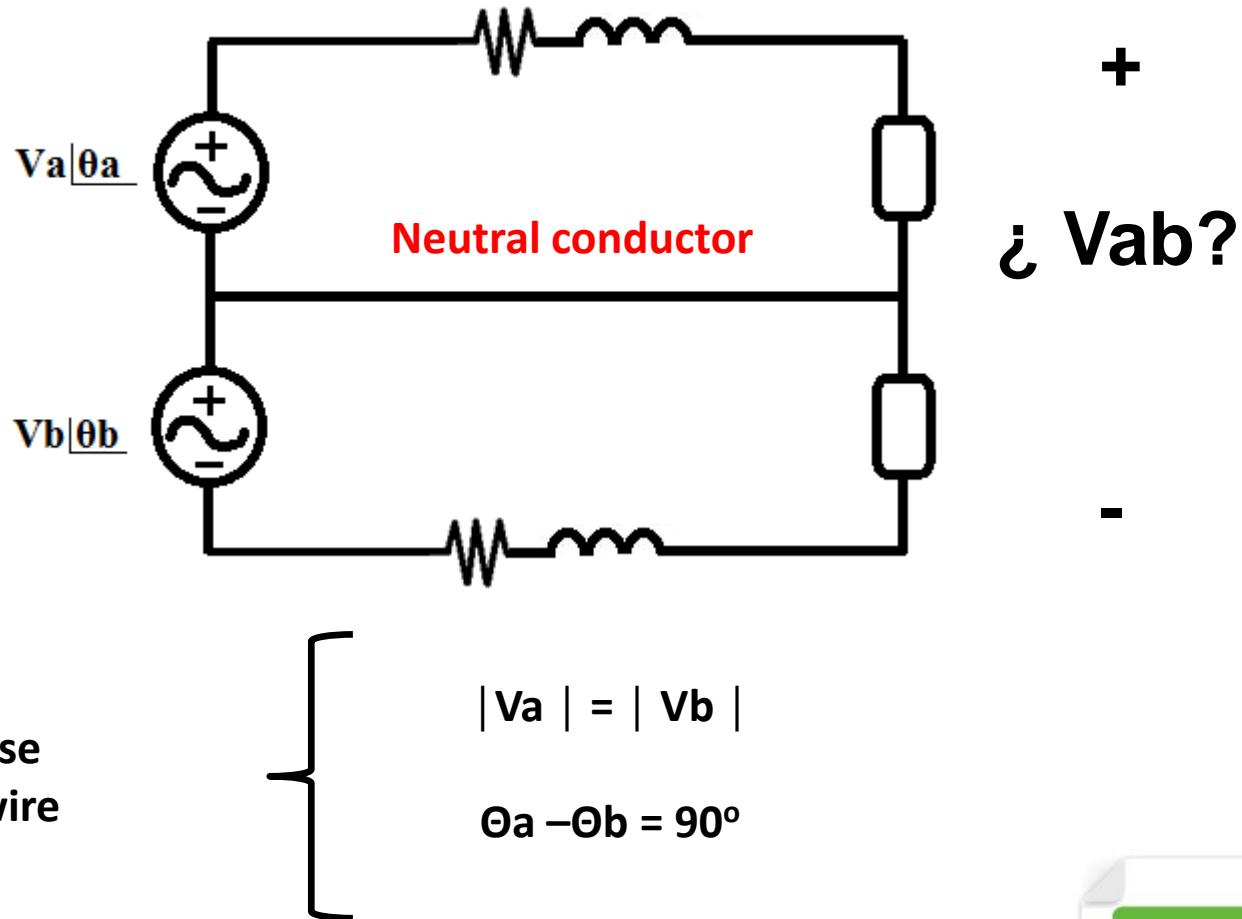


Three-phase circuits

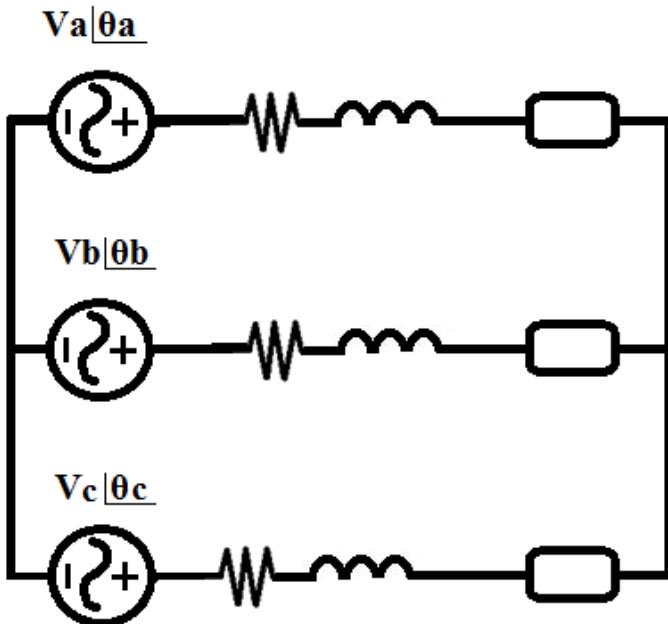


Three-phase three-wire

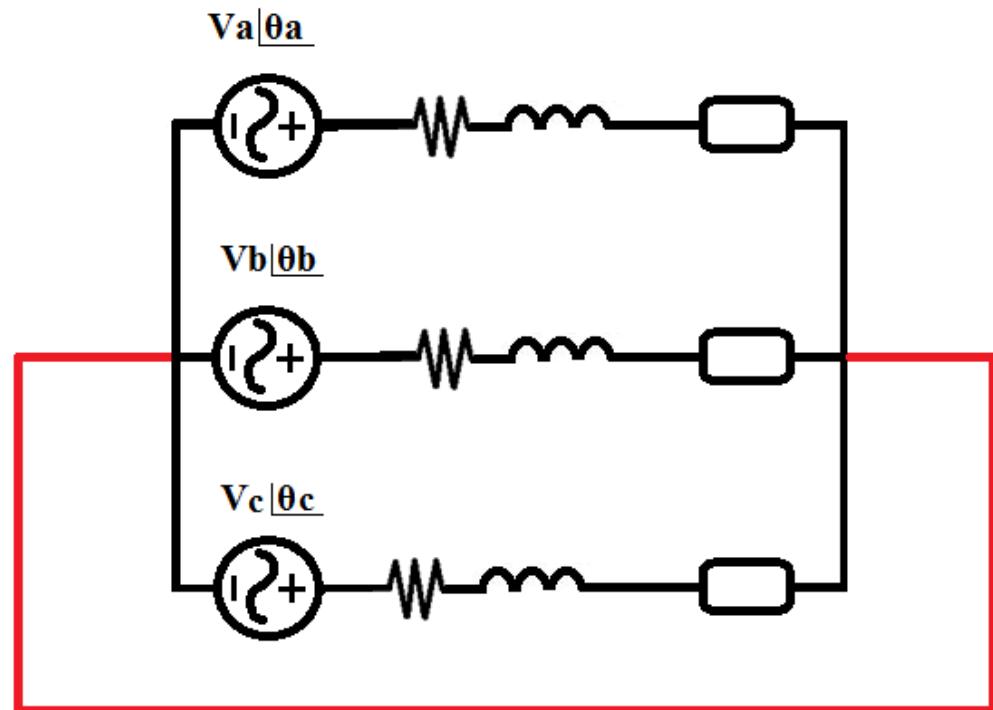Substations (RST)
Motors (UVW)
Transformers (XYZ)



Three-phase four-wire
Neutral conductor

Three-phase circuits

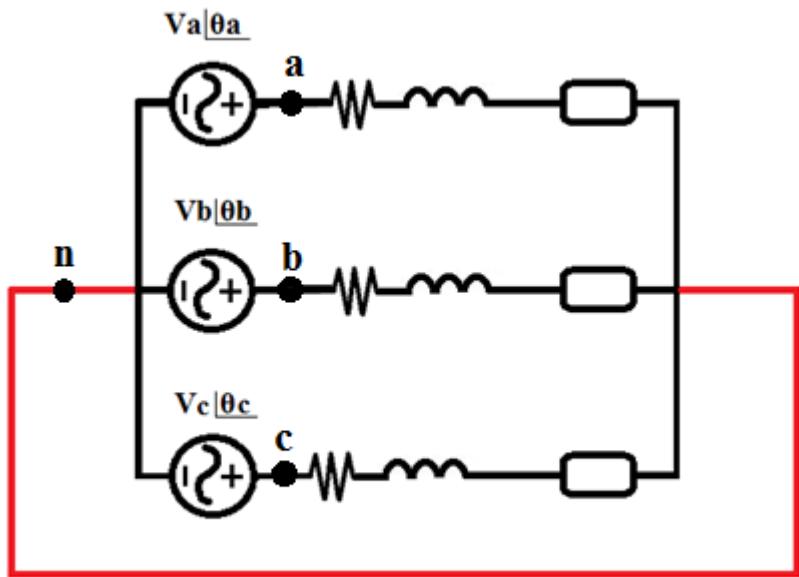

Neutral conductor

$$|V_{an}| = |V_{bn}| = |V_{cn}|$$


Positive sequence Negative sequence

$$\begin{aligned}\Theta_{an} &= \Theta^\circ \\ \Theta_{bn} &= \Theta^\circ - 120^\circ \\ \Theta_{cn} &= \Theta^\circ + 120^\circ\end{aligned}$$


$$\begin{aligned}\Theta_{an} &= \Theta^\circ \\ \Theta_{bn} &= \Theta^\circ + 120^\circ \\ \Theta_{cn} &= \Theta^\circ - 120^\circ\end{aligned}$$

If the voltage source have the same amplitude and frequency ω and they are out of phase with each other by 120° , the voltages are said to be balanced.

Three-phase circuits

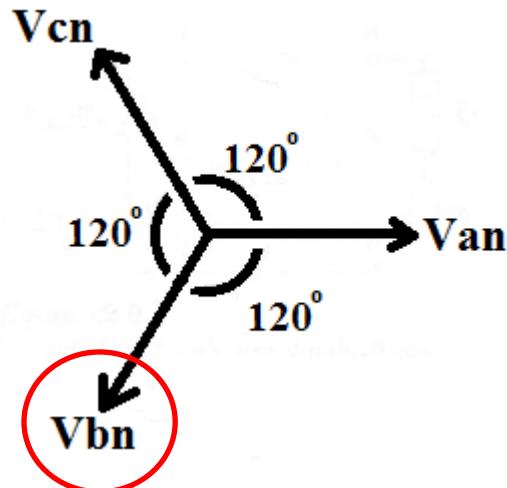

Positive sequence

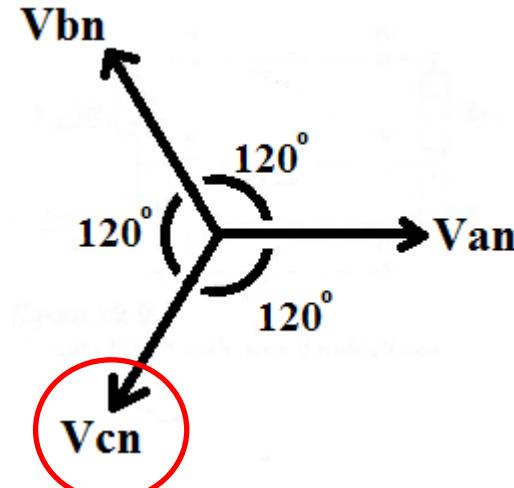

Negative sequence

$$|V_{an}| = |V_{bn}| = |V_{cn}|$$

Positive sequence (ABC)

$$\Theta_{an} = \Theta^\circ$$

$$\Theta_{bn} = \Theta^\circ - 120^\circ$$

$$\Theta_{cn} = \Theta^\circ + 120^\circ$$


Negative sequence (ACB)

$$\Theta_{an} = \Theta^\circ$$

$$\Theta_{bn} = \Theta^\circ + 120^\circ$$


$$\Theta_{cn} = \Theta^\circ - 120^\circ$$

Three-phase circuits

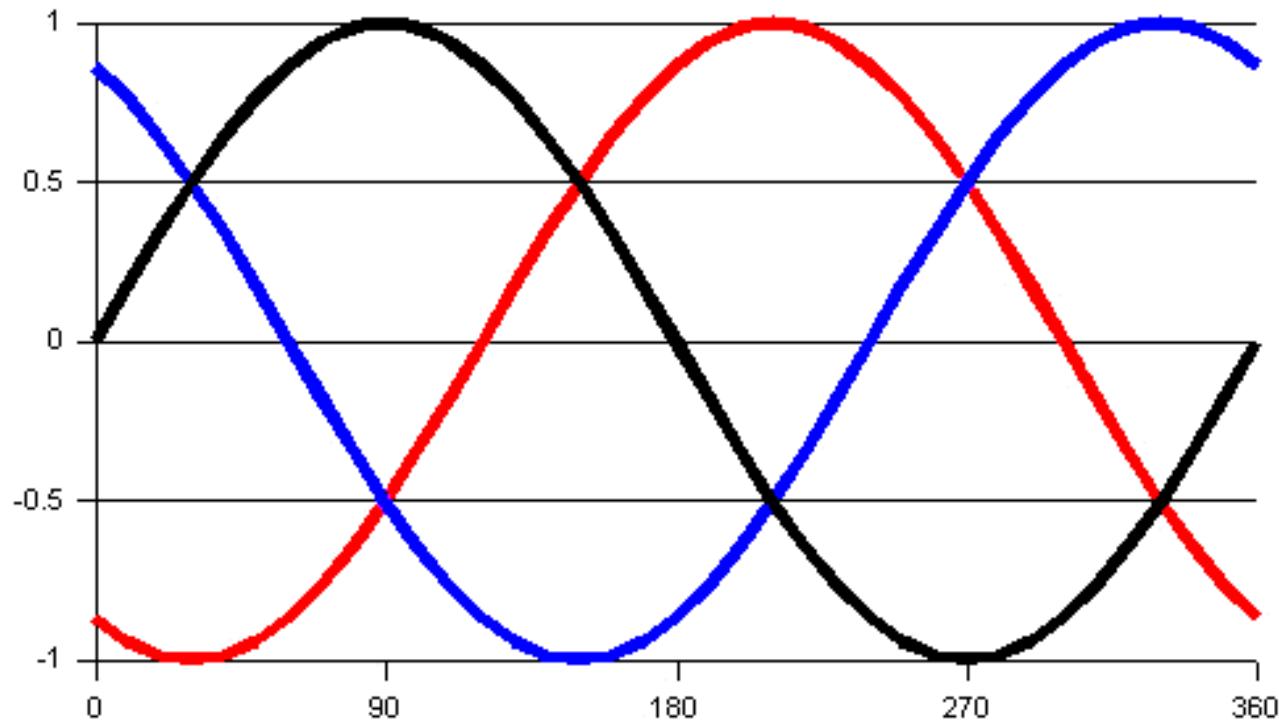


C O N S T R U I M O S F U T U R O

Three-phase circuits

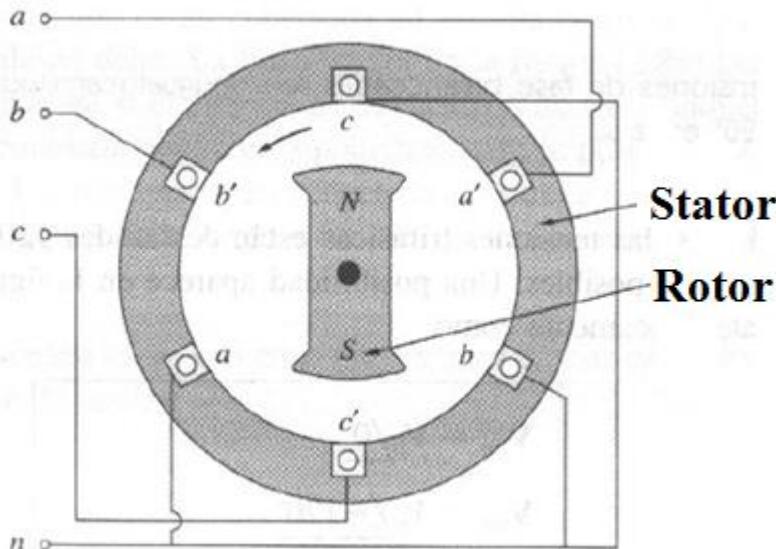

Source [Sadiku]

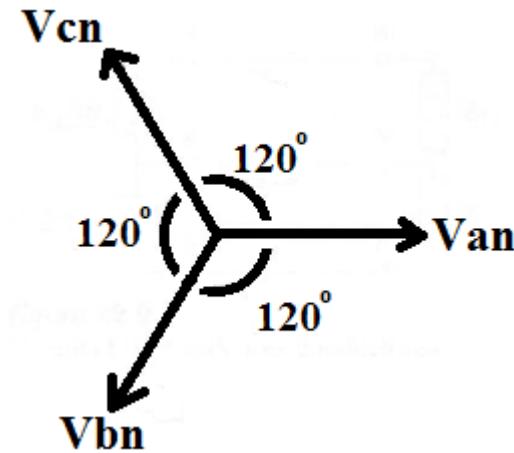


¿How much these voltages add?


Excercise:

$$\begin{aligned} V_{an} &= 100 \angle 170^\circ \text{ Sec (+)} & \text{¿}V_{cn}\text{?} \\ V_{nc} &= 50 \angle -30^\circ \text{ Sec (-)} & \text{¿}V_{an}\text{?} \end{aligned}$$

Three-phase circuits

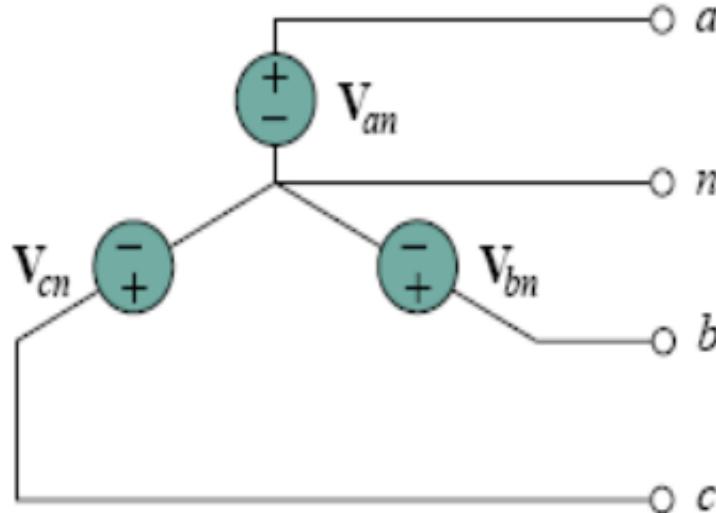


Wye-connected source

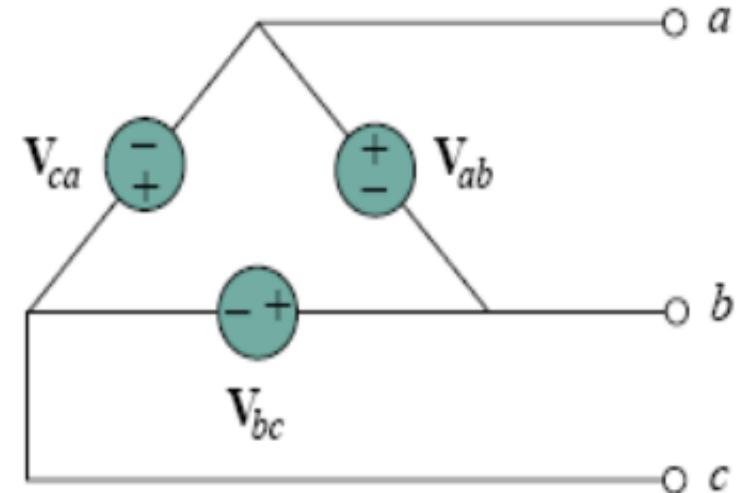

Delta-connected source


Three-phase circuits

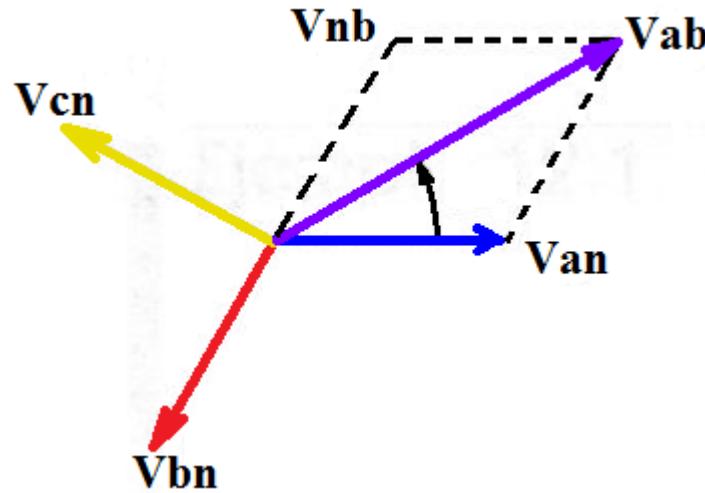

$$VL = \sqrt{3} V_{ph} \angle -30^\circ \text{ Sec (+)}$$
$$VL = \sqrt{3} V_{ph} \angle -30^\circ \text{ Sec (-)}$$

Excercise:
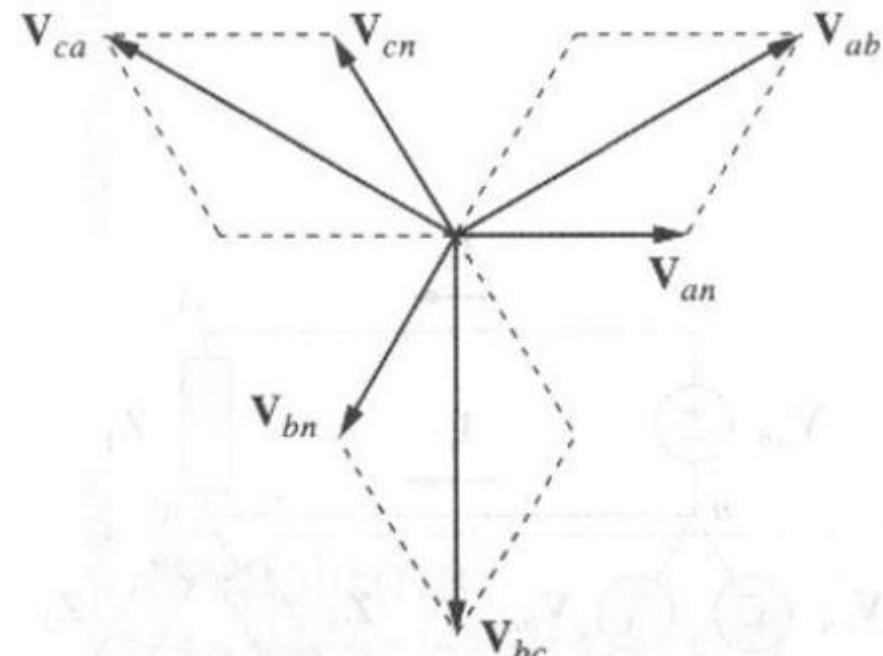
$$V_{bn} = 30 \angle -10^\circ \text{ Sec (+)} \quad ?V_{ca}?$$
$$V_{ca} = 400 \angle 20^\circ \text{ Sec (-)} \quad ?V_{nb}?$$



Three-phase circuits

- The power is generated and distributed in three-phase circuits.
- Single-phase voltages are obtained from three-phase systems. (ex: residential electrical installations)
- Less transmission losses.


C O N S T R U I M O S F U T U R O

Universidad
Industrial de
Santander



Homework

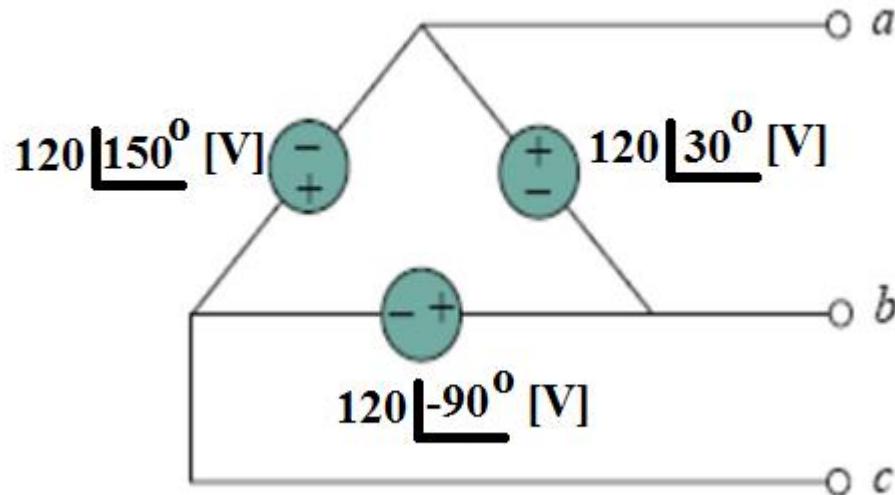Find the values of the equivalent wye-connected sources:



Thank you for your attention

C O N S T R U I M O S F U T U R O

Universidad
Industrial de
Santander

