

1.2 Three-phase circuits

JUAN MANUEL REY LÓPEZ
Profesor Auxiliar
juanmrey@uis.edu.co

Escuela de Ingenierías Eléctrica, Electrónica y de
Telecomunicaciones
Universidad Industrial de Santander




I - 2015

C O N S T R U I M O S F U T U R O

Universidad
Industrial de
Santander



Polyphase circuits

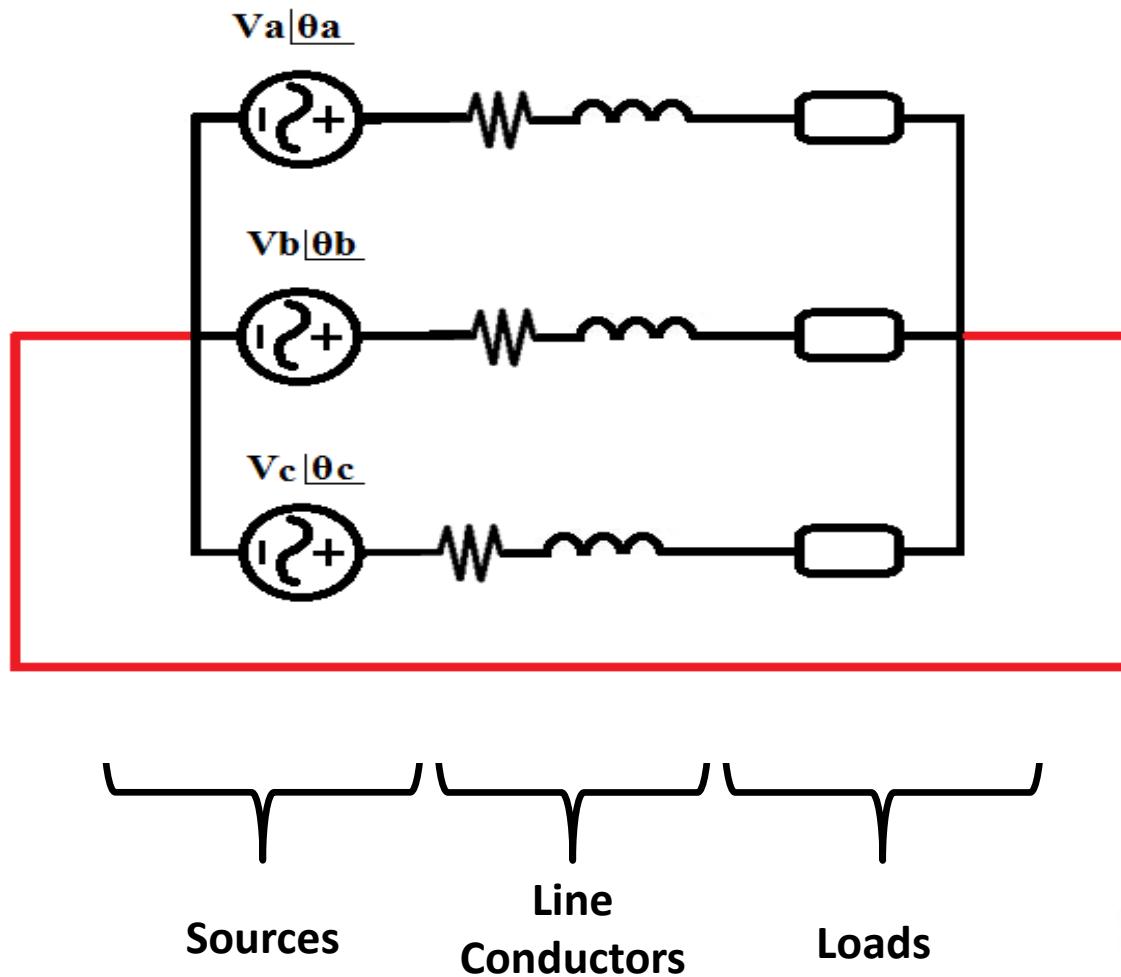


C O N S T R U I M O S F U T U R O

Universidad
Industrial de
Santander




Homework

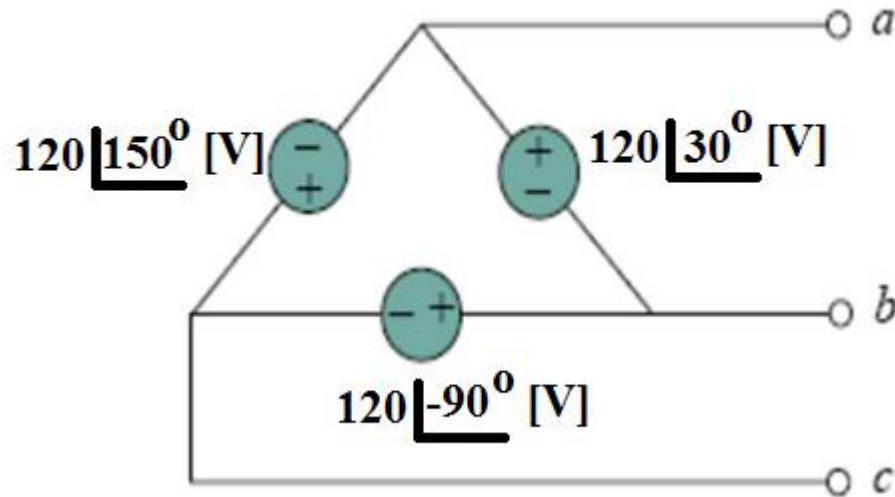
Find the values of the equivalent wye-connected sources:




Loads

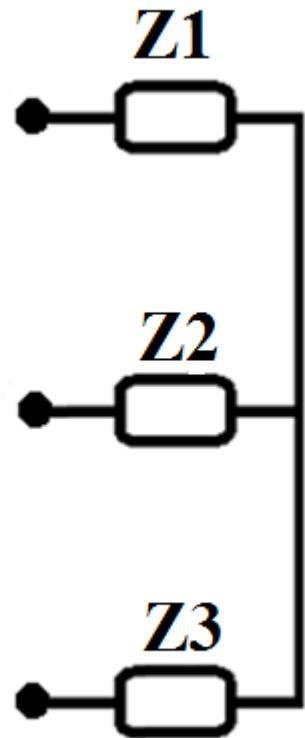

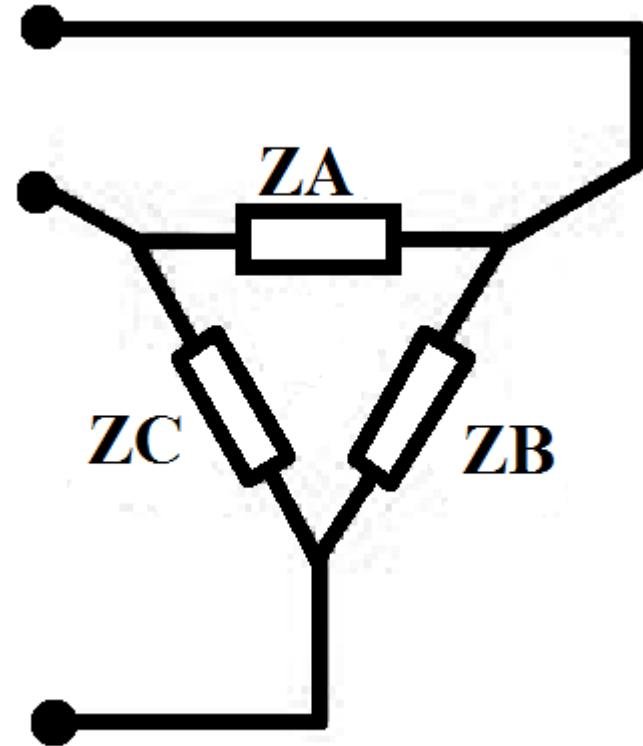
$$Z_1 = \frac{Z_A * Z_B}{Z_A + Z_B + Z_C}$$




Loads

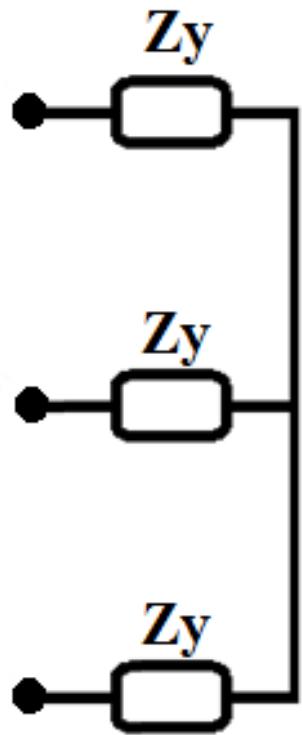

$$Z_y = \frac{Z\Delta}{3}$$

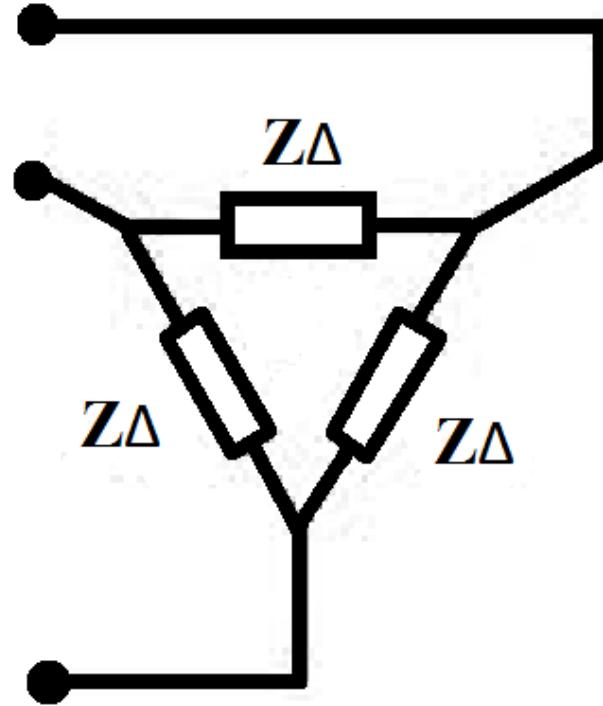


Polyphase circuits

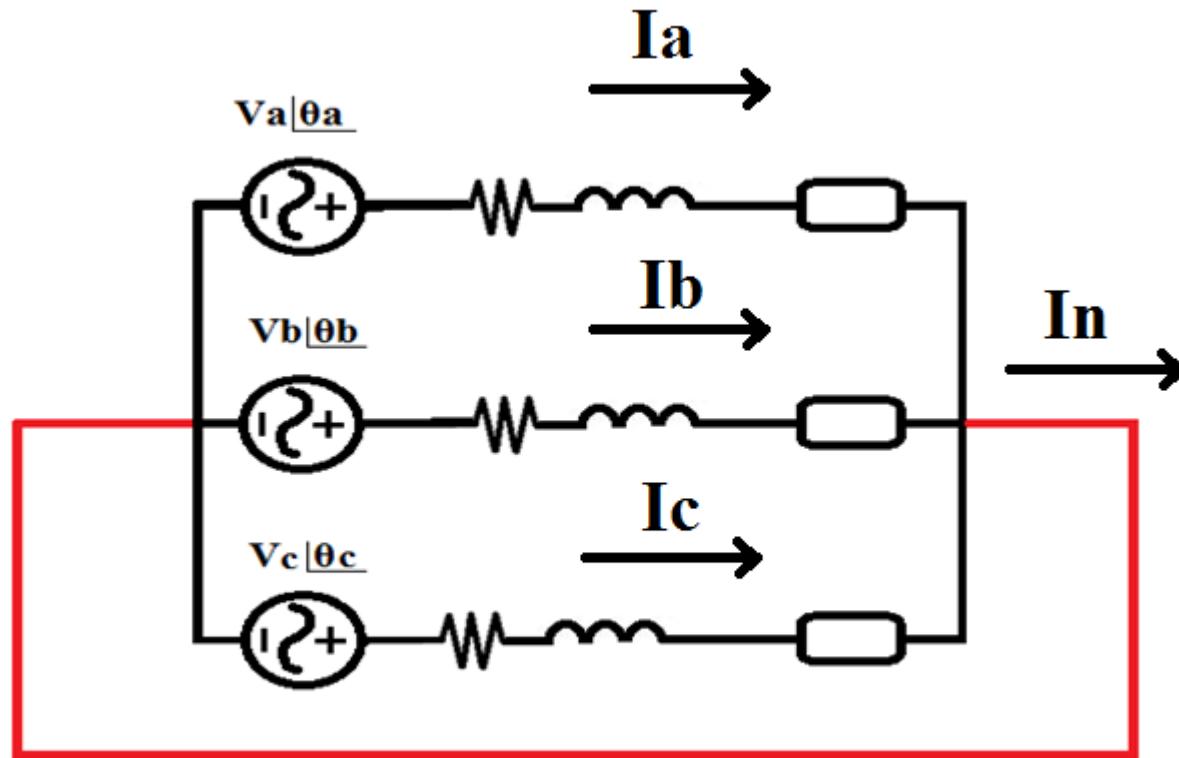

Always (KCL) $I_n = I_a + I_b + I_c$
If the loads are unbalanced?


Line and phase currents

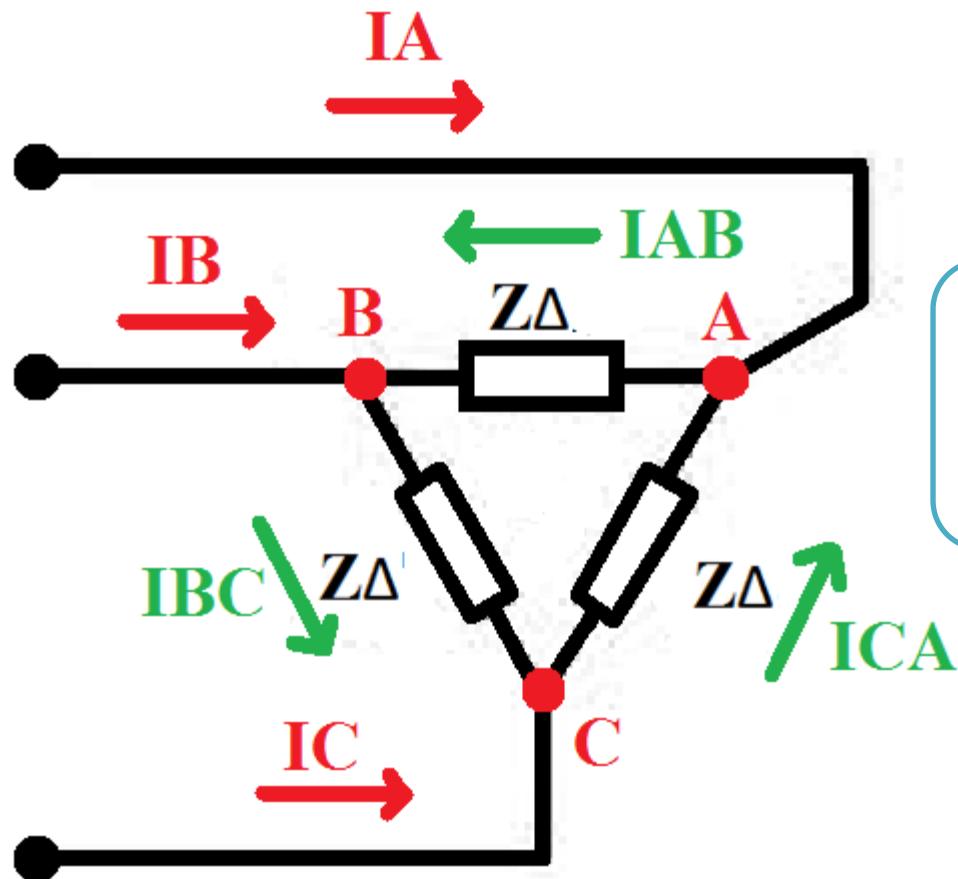

$$I_L = \sqrt{3} I_{PH} \angle -30^\circ \text{ Sec (+)}$$

$$I_L = \sqrt{3} I_{PH} \angle 30^\circ \text{ Sec (-)}$$

Polyphase circuits

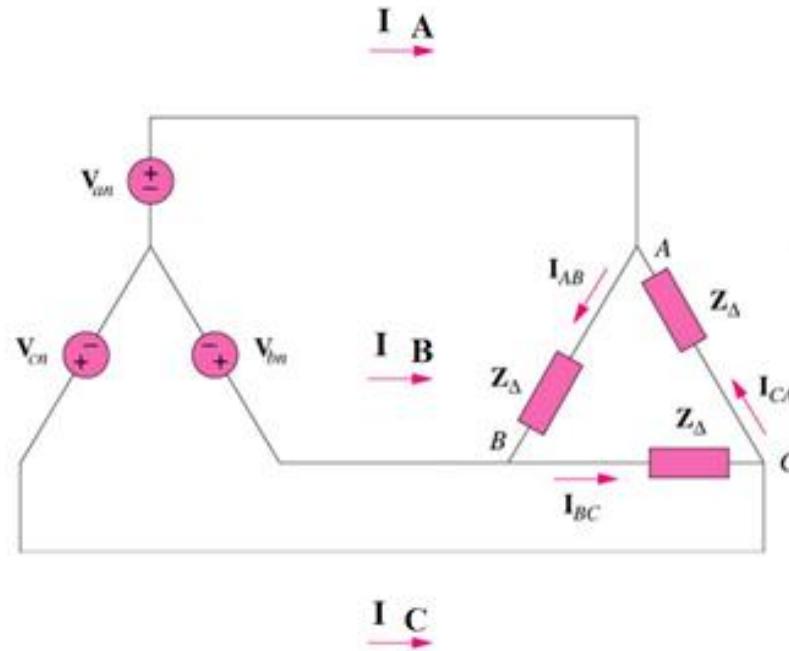

Find I_{AB} and I_B if $V_c = 20 \angle 15^\circ [V]$

Wattmeter

An instrument for measuring the electric power.



Before class: find a video ([URL](#)) about how to use a wattmeter.

Wattmeter

An instrument for measuring the electric power.



$$W_x = V * I * \cos (\theta_V - \theta_I)$$

Homework

How does the two-meter wattmeter method works?

Thank you for your attention

C O N S T R U I M O S F U T U R O

Universidad
Industrial de
Santander

