

# Presentation

JUAN MANUEL REY LÓPEZ  
Profesor Auxiliar  
[juanmrey@uis.edu.co](mailto:juanmrey@uis.edu.co)

Escuela de Ingenierías Eléctrica, Electrónica y de  
Telecomunicaciones  
Universidad Industrial de Santander



I - 2015

C O N S T R U I M O S F U T U R O



# WELCOME

## Electrical Circuits II (27134) – B1 B2

- Theory: Wednesday 8-10 am  
                      Friday         8-10 am
- Lab:           Tuesday       8-10 am (B1)  
                     Thursday      8-10 am (B2)

**PROFESSOR: JUAN MANUEL REY**  
**[juanmrey@uis.edu.co](mailto:juanmrey@uis.edu.co)**

C O N S T R U I M O S F U T U R O



# WELCOME

**Office: 204 LP – Third door on the left**

**PROFESSOR: JUAN MANUEL REY**  
**[juanmrey@uis.edu.co](mailto:juanmrey@uis.edu.co)**

**Questions?**

C O N S T R U I M O S F U T U R O

Universidad  
Industrial de  
Santander



# WELCOME

**Why in english?**

**Why with moodle?**


**Who are you?**

C O N S T R U I M O S F U T U R O


Universidad  
Industrial de  
Santander



# TOPICS

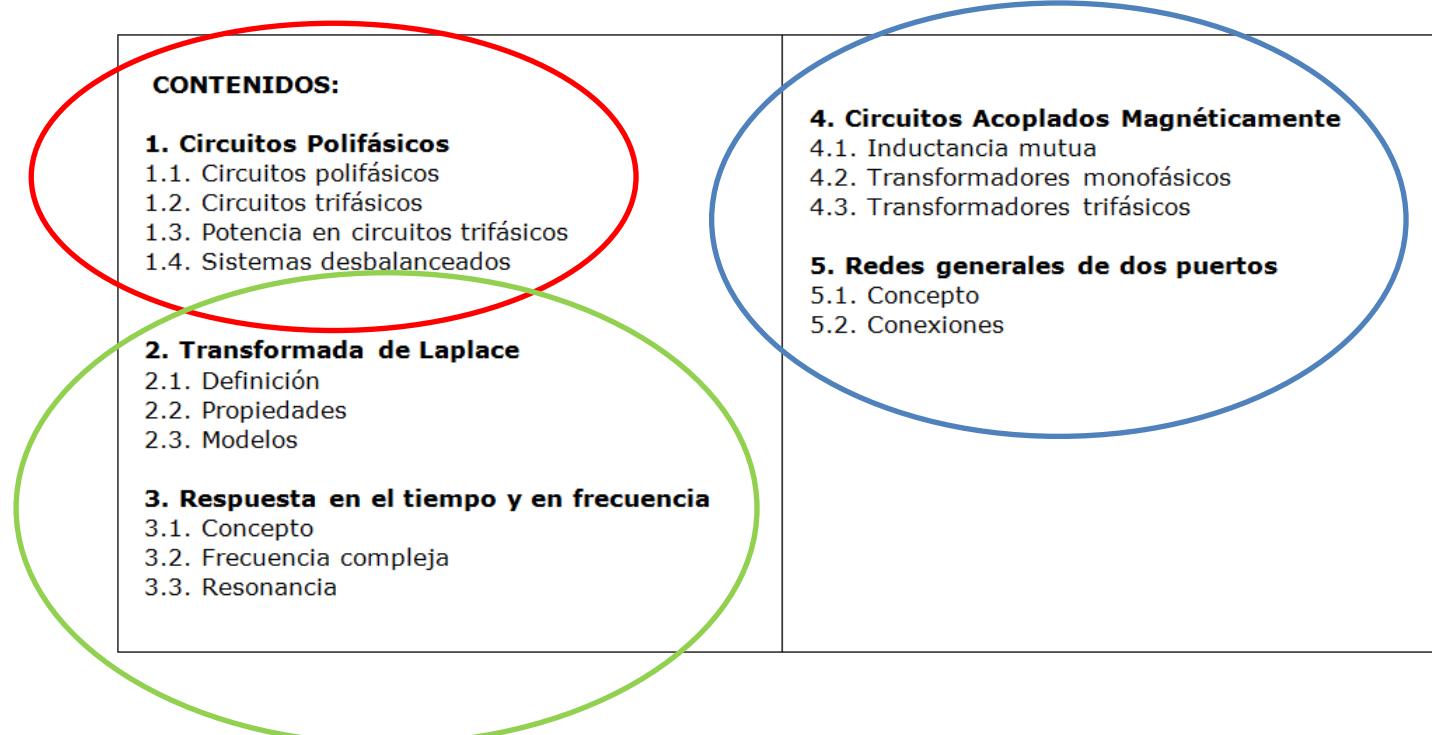

# EVALUATIONS

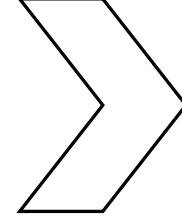- Partial evaluation 1 (17 April)
  - Partial evaluation 2 (22 May)
  - Partial evaluation 3 (27 July)
- 
- 80%
- 
- Lab -> 15%
  - Quizzes – homeworks-> 5%
- 
- Estimated effort : 4 hours/week + 2 hours/week (?)

C O N S T R U I M O S F U T U R O



# PREREQUISITES

- Domain Kirchhoff's Laws!
- Domain Ohm's law.
- Solve multivariable linear equations
- Know how to use your calculator




Let's  
see!

# Example 1

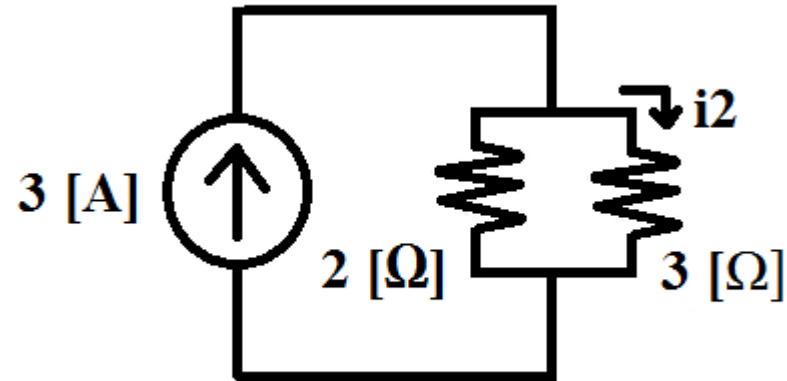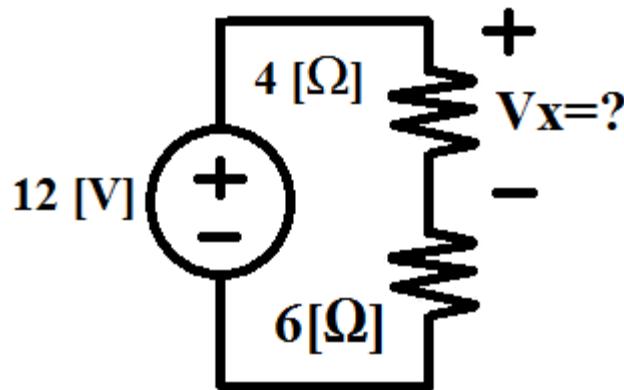

Find  $V_X$   
and  $I_2$

# Example 2

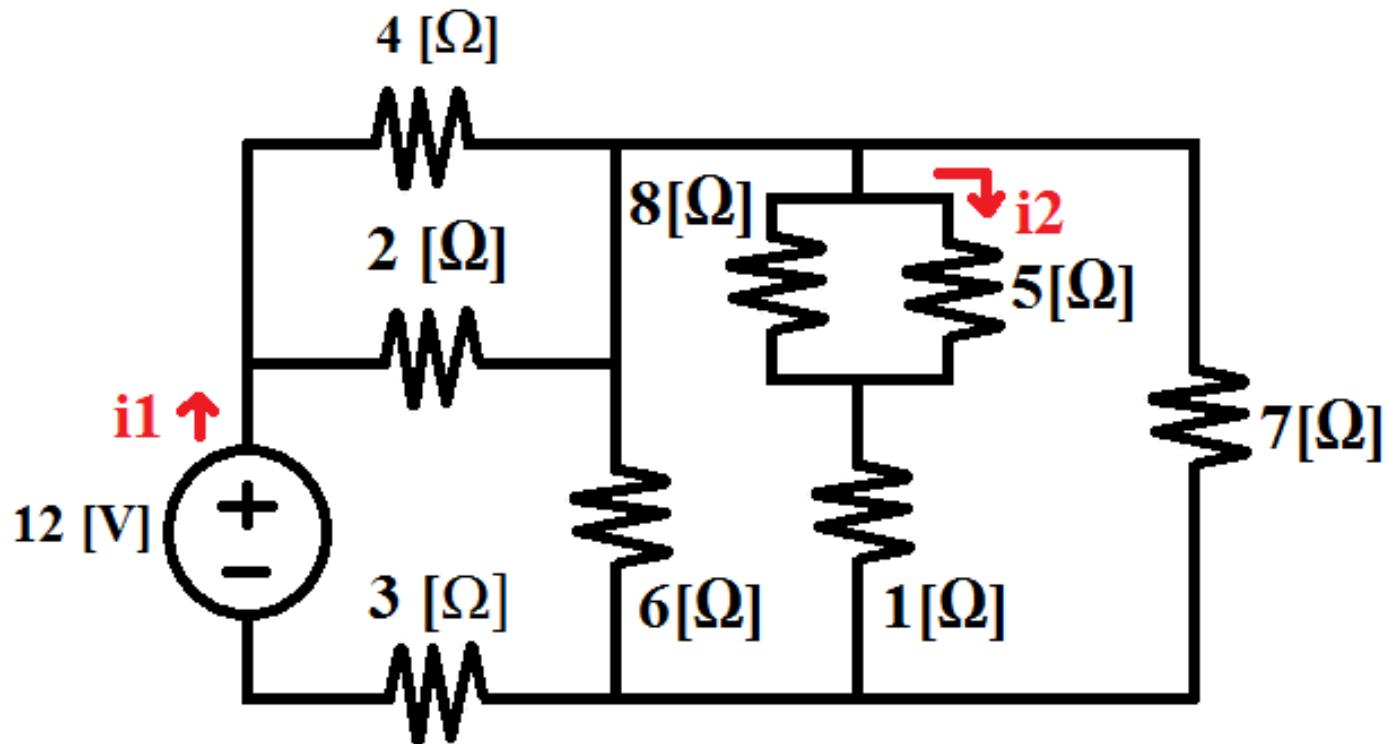

Find  $i_1$   
and  $i_2$

# Example 3

$$15X = \frac{1 - X^2}{\sqrt{e^X}}$$



Find X

# Example 4

$$12 = 11V + 3W + 4X - 8Y + 11Z$$

$$17 = 12V + 32W + 19X + 6Y - Z$$

$$-4 = V - 6W + 2X + 6,7Y - 2Z$$

$$0 = 1,3V - 8W - 3,2X + 5Y + 14Z$$

$$10,2 = 5V + 2,3W + X + 6Y - 12,6Z$$



Solve the system!

# **Thank you for your attention**

C O N S T R U I M O S F U T U R O

Universidad  
Industrial de  
Santander

